

Associating bond graph junctions with series/parallel structures






Exercise solution: sorted tables

Summarized solution:

- **0 junctions** (shared effort) corresponds to:
 - parallel connections of electrical elements
 - series connected of mechanical devices
- **1 junctions** (shared flow) correspond to:
 - series connection of electrical elements (loop of share current)
 - parallel connection of mechanical devices (several forces/devices acting on the same velocity point)

Important observation: the association is flipped between mechanics and electricity!

Reminder: BG elements in electrical and mechanical domains

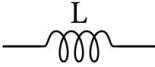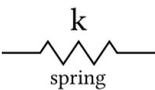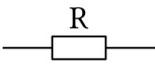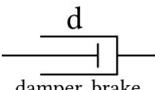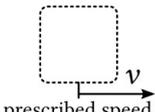	Bond graph	Electricity	Mechanics (translation)
1	$\frac{e}{f} \nearrow I$		 inertia
2	$\frac{e}{f} \nearrow C$		 spring
3	$\frac{e}{f} \nearrow R$		 damper, brake
4	Se $\frac{e}{f} \nearrow$		
5	Sf $\frac{e}{f} \nearrow$		 prescribed speed

Warning: a capacitor C is equivalent to a spring $k=1/C$!

(no such problem for I and R : $L=m$ and $R=d$)

Association 1: a single 0/1 junction with series/parallel structure

Bond graph	Electricity	Mechanics (translation)
<p>1 Common effort</p>	<p>Common voltage: //</p>	<p>Common force: series</p>
<p>2 Common flow</p>	<p>Common current: series</p>	<p>Common speed: ~//</p>

Notice that dampers or spring connected to an absolute speed (i.e. not to a relative speed, using a 0 junction as explained in the M2 example) *needs to be grounded* on the other side.

Association 2: combined 0/1 junc. with series/parallel structures

Associate each bond graph with its corresponding electrical circuit or mechanical system.

Bond graph	Electricity	Mechanics (translation)
<p>1</p>	<p>L in // with (R-C in series)</p>	<p>F applied to both m and k//d</p>
<p>2</p>	<p>L in series with R//C</p>	<p>F shared between m and d-k</p>